

ENGR 101
Intro to Engineering:
Week 5

Section V: Resistance

- A circuit is composed of two or more devices connected by a conductor

Circuit elements:

emf

resistors

capacitors

inductors

Energy type:

source

sink

store

convert

We will focus on resistance since all devices and conductors oppose the flow of current: they have electrical resistance or impedance ... caused by free electrons colliding with the lattice of atoms of the conductors.

Resistor


- A circuit element specifically for providing resistance is called a resistor. The ratio of the electric pressure \mathcal{E} (voltage) to the current (i):

Georg Ohm
1789-1854
Ohm's Law

$$\mathcal{E} / i \equiv \text{Volts/Amperes} = \text{Ohms } [\Omega] \text{ or } [V/A]$$



resistor
symbol

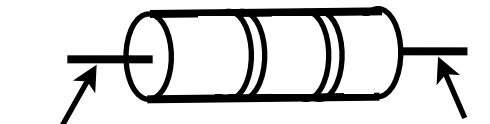

lead solid paper resistor lead


Carbon paper
composite
2.2 Ω to 1M Ω

Adjustable
resistors -
potentiometers
rheostats

Resistors absorb electrical energy (sink) and dissipates it as heat. The resistors are rated by their resistances (ohms) and power rating (watts).

Ohm's Law

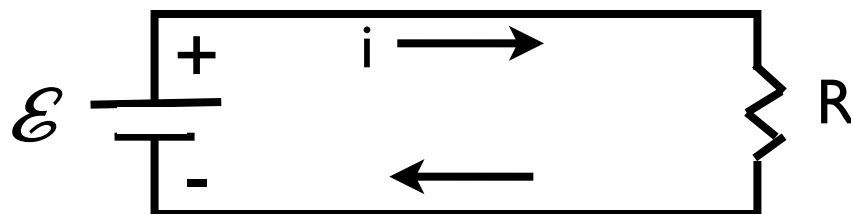- Consider the flow of electrons in the following system of conductors or circuit.



Ohm's Law : the potential difference across a conductor is directly proportional to the current.


Mathematically:

$$V = R I$$

constant of proportionality

example:
 $10\text{V}/10\text{A} = 1\Omega$

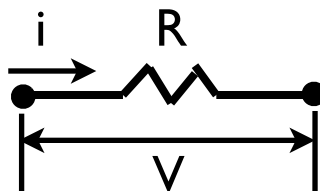
example:
 $10\text{V}/20\text{A} = 0.5\Omega$



Need 2 points in the circuit to measure the V - the potential difference

Resistors in Series

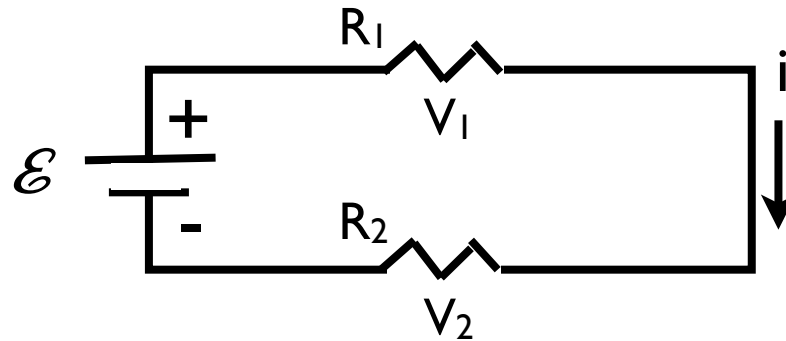- When two or more resistors are connected such that there is only one conducting path between them they are said to be in a series arrangement.



In a series circuit the voltage drop across each resistor is in accordance with Ohm's Law, e.g. $V_1 = -i R_1$ and $V_2 = -i R_2$

Kirchoff's Voltage Law (KVL): the sum of voltage changes around a closed loop is zero. Mathematically: $\sum V = 0$

Equivalent Resistance

- Using Kirchoff's Voltage Law

$$\mathcal{E} - V_1 - V_2 = 0 \quad \text{or} \quad \mathcal{E} = V_1 + V_2$$

- Substituting Ohm's Law

$$\mathcal{E} = i R_1 + i R_2 = i (R_1 + R_2)$$

Dividing by i and applying Ohm's Law again yields the effective or equivalent resistance of the two resistors in series:

$$\mathcal{E}/i = \boxed{R_s = R_1 + R_2}$$

More generally for any number of resistors in series:


'series resistance'

$$\boxed{R_s = \sum R}$$

Equivalent Circuit


- What is the voltage that must be furnished by the battery to force 0.25A through the following circuit?

Simplify the circuit

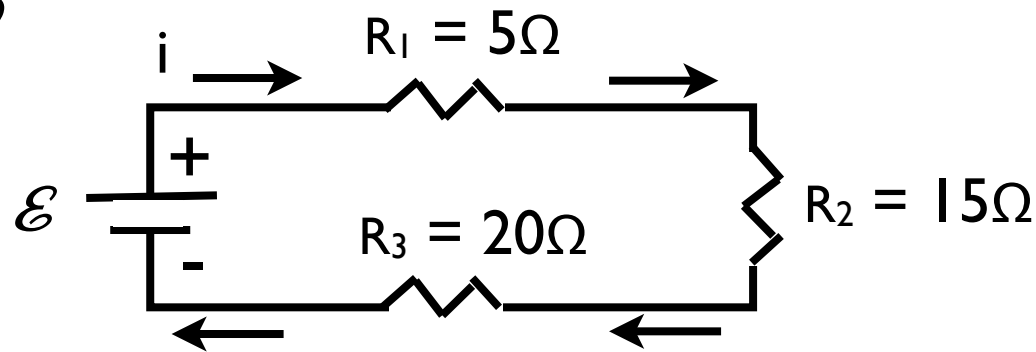

The equivalent resistance is: $R_s = \sum R = R_1 + R_2 + R_3 = 5 + 15 + 20 = 40 \Omega$

The 'equivalent' circuit

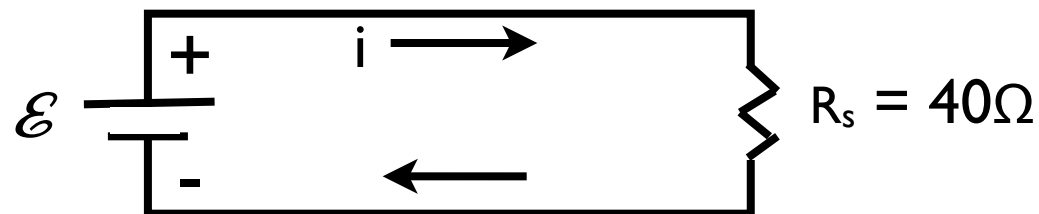


Using KVL and Ohm's Law: $\sum V = 0$ or $\mathcal{E} - V_s = 0$
and $\mathcal{E} - iR_s = 0$, solving for: $\mathcal{E} = 0.25\text{A} \cdot 40\Omega = 10\text{V}$

Resistors in Parallel

- When two or more resistors are connected across the same emf they are said to be in a parallel arrangement.

Simplify the circuit

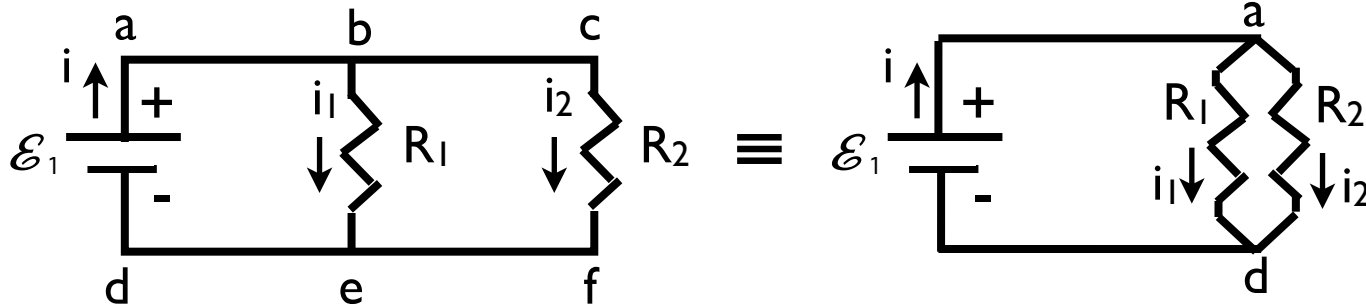

The 'equivalent' circuit

Def.: A node or junction is a point of connection of two or more circuit elements - a node may not be a single point but a collection of point on a conductor that are electrically identical.

Voltage across resistors in parallel is constant but the current through each resistor is different.

Kirchoff's Current Law


- Kirchoff's Current Law (KCL): requires that the sum of currents at any node sums to zero.

Mathematically:

$$\sum i = 0$$

Convention: current flowing into a junction is positive, current flowing away from a junction is negative.

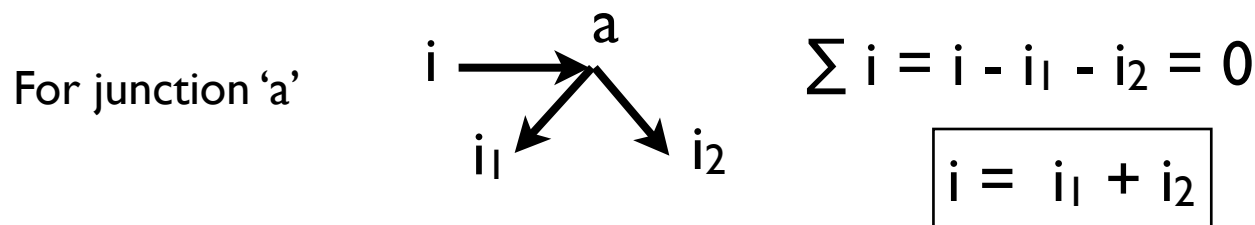For the given two resistor circuit, Ohm's Law yields: $i_1 = V_{ad}/R_1$ and $i_2 = V_{ad}/R_2$ where V_{ad} is the potential across nodes a & d. The total current is found by using KCL.



Equivalent Parallel R

- Apply Ohm's Law to the KCL results:

$$i = i_1 + i_2 = V_{ad}/R_1 + V_{ad}/R_2 = V_{ad} (1/R_1 + 1/R_2)$$

Dividing by V_{ad} and applying Ohm's Law again yields:

$$i / V_{ad} = \boxed{1/R_p = 1/R_1 + 1/R_2}$$

More generally for any number of resistors in parallel:

Invert these
formula for R_p

$$\boxed{1/R_p = \sum 1/R}$$

For two resistors in parallel:


$$1/R_p = (R_1 + R_2) / R_1 R_2$$

For three resistors in parallel:

$$1/R_p = [R_3(R_1 + R_2) + R_1 R_2] / R_1 R_2 R_3$$

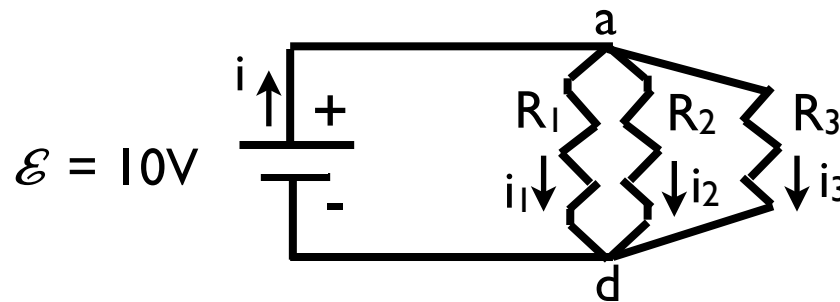Examples

- For three resistors connected in parallel




$$\begin{aligned}R_1 &= 5\Omega \\R_2 &= 15\Omega \\R_3 &= 20\Omega\end{aligned}$$

$$\begin{aligned}\frac{1}{R_p} &= \sum \frac{1}{R} \\&= \frac{1}{5} + \frac{1}{15} + \frac{1}{20} \\&= \frac{12}{60} + \frac{4}{60} + \frac{3}{60} \\&= \frac{19}{60} \\R_p &= \frac{60}{19} = 3.158\Omega\end{aligned}$$

'parallel' resistance


The 'equivalent' circuit is:

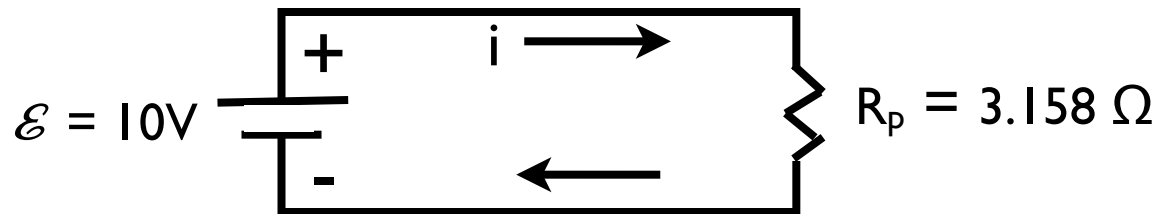

$$\text{Using Ohm's Law: } i = V_{ad}/R_p = 10\text{V} / 3.158\Omega = 3.167\text{A}$$

Mixed Circuits

- Series and parallel resistors

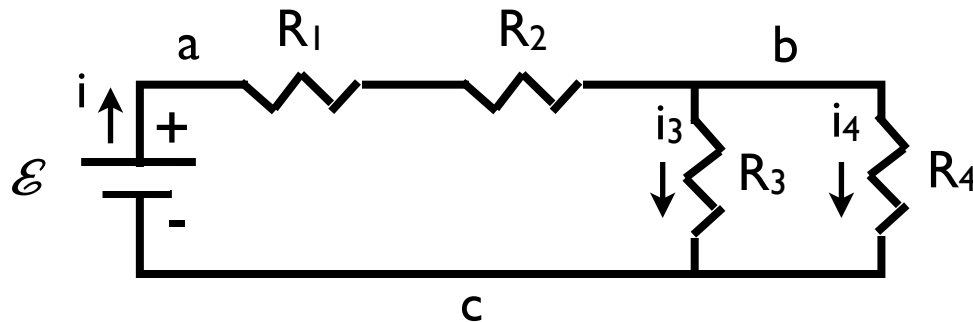


Combine R_1 and R_2 in series and R_3 and R_4 in parallel.

$$R_s = R_1 + R_2$$

$$R_p = R_3 R_4 / (R_3 + R_4)$$

$$R_e = R_s + R_p$$

'equivalent' resistance

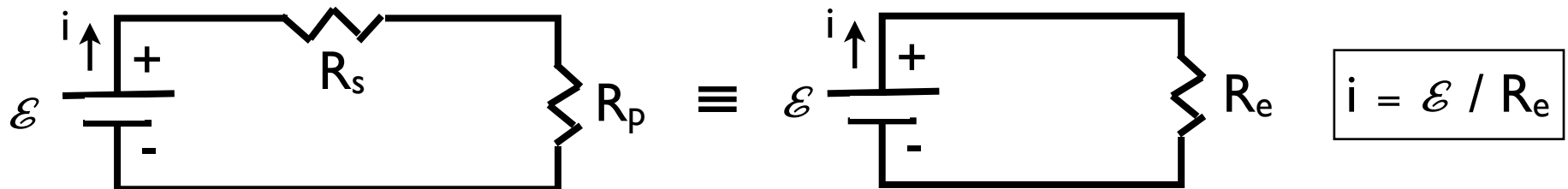

$$V_s = i R_s$$

$$V_p = i R_p$$

$$V_1 = i R_1$$

$$V_2 = i R_2$$

$$i_3 = V_p / R_3$$

$$i_4 = V_p / R_4$$